

### Practical: - 2:1 MUX using logic gate and transmission gate



